

# Recap

Tuesday, February 9, 2016 5:47 PM

Quantum fluid model: charged bosons coupled to fm field  $-\frac{1}{nq^2} \nabla \left( \frac{\Lambda}{2} \vec{j}^2 \right)$

$$i\hbar \partial_t \psi = \left\{ \frac{1}{2m} \left[ -i\hbar \vec{\nabla} - q \vec{A} \right]^2 + qU \right\} \psi$$

↳ Wavefunction:  $\psi \sim \sqrt{n} e^{i\theta}$ ,  $q$  = charge carrier dty

↳ 1st London equation  $\frac{\partial}{\partial t} (\Lambda \vec{j}) = \vec{E} - \frac{1}{nq} \vec{\nabla} \left( \frac{\Lambda}{2} \vec{j}^2 \right)$

↳  $\Lambda = \frac{m}{q^2 n}$  ~ inductance  $\sqrt{\frac{m}{\Lambda}}$  ~ penetration depth

↳ Charge current  $\vec{j} \sim qn \left[ \frac{\hbar}{m} \vec{\nabla} \theta - \frac{q}{m} \vec{A} \right]$



↳ Fluxoid quant.  $\oint_C (\Lambda \vec{j}) \cdot d\vec{l} + \underbrace{\oint_C \vec{B} \cdot d\vec{s}}_{\Phi_{\text{ext}}} \in \Phi_0 \times \mathbb{Z}$   $\Phi_0 = \frac{h}{q} = \frac{h}{2e}$  flux quantum

↳ Flux-phonon  $\partial_t \theta = -\frac{qU}{\hbar}$

# Josephson relation

Saturday, February 6, 2016

6:28 PM

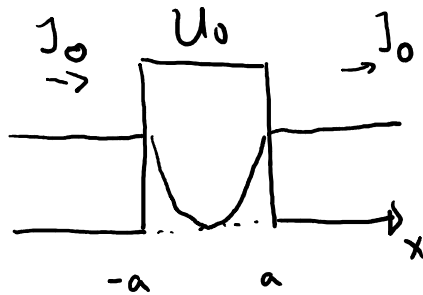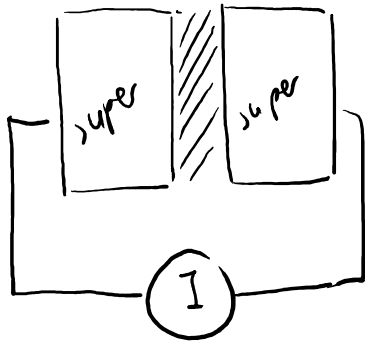

- \* We consider the superconducting current that can be established between two superconductors through a thin insulator
- \* We model this as a quantum tunnel process through a potential barrier for the Cooper pairs, which come with energy  $E \ll U_0$
- \* We seek stationary solutions in absence of flux. We start w.  $\vec{A} = 0$

$$E\psi = \left[ \frac{\hbar^2}{2m^*} (-i\hbar \nabla - g\vec{A})^2 + V_0 \right] \psi$$

- \* Outside the barrier we assume a constant density and uniform current

$$\wedge J_0 \sim \frac{\hbar}{g} \frac{d\theta}{dx} \quad \rightarrow \quad \begin{aligned} \psi(x < -a) &\sim \sqrt{n_L} \exp(i\theta_L(x)) \\ \psi(x > +a) &\sim \sqrt{n_R} \exp(i\theta_R(x)) \end{aligned}$$

- \* Between boundaries

$$\frac{\hbar^2}{2m^*} \frac{d^2\psi}{dx^2} = (U_0 - E)\psi \quad \rightarrow \quad \psi(x) = C_1 \cosh(x/\xi) + C_2 \sinh(x/\xi) \quad \xi = \sqrt{\frac{\hbar^2}{2m(U_0 - E_0)}}$$

property of insulator, not penetrat. depth

# Josephson relation (2)

Sunday, February 7, 2016 4:32 PM

Matching boundary conditions  $\psi(-a) = \sqrt{n_L} e^{i\theta_L}$ ,  $\psi(a) = \sqrt{n_R} e^{i\theta_R}$

$$C_1 = \frac{\sqrt{n_L} e^{i\theta_L} + \sqrt{n_R} e^{i\theta_R}}{2 \cosh(a/\xi)}, \quad C_2 = \frac{\sqrt{n_R} e^{i\theta_R} - \sqrt{n_L} e^{i\theta_L}}{2 \sinh(a/\xi)}$$

Notice that by defining  $J_c$  with  $(-g^*/\hbar)$ , we invert the order of phases \*

$$J_s = \frac{g^*}{m^*} \text{Re}(-\psi^* i \hbar \nabla \psi) = \frac{g^* \hbar}{m^*} \text{Im}(C_1^* C_2) = J_c \sin(\theta_L - \theta_R) \text{ uniform along junction}$$

$$J_c = \textcircled{-} \frac{g^* \hbar}{2m^*} \frac{\sqrt{n_L n_R}}{\sinh(2a/\xi)} > 0 \text{ is the critical current below which tunnelling is sup.}$$

More generally, provided  $\vec{\nabla} \times \vec{A} \times \vec{B} = 0$ , we can write

$$\vec{J} = J_c \sin \varphi \text{ with the gauge invariant phase}$$

$$\varphi = \theta_L - \theta_R - \frac{2\pi}{\Phi_0} \int_L^R \vec{A} \cdot d\vec{l}$$

# Josephson relation (3)

Sunday, February 7, 2016 4:45 PM

\* Phase-voltage relations  $\frac{\partial}{\partial t} \varphi = \frac{\partial}{\partial t} \theta_L - \frac{\partial}{\partial t} \theta_R - \frac{2\pi}{\Phi_0} \int_L^R \frac{\partial \bar{A}}{\partial t} \cdot d\bar{l}$   $\Phi_0 = \frac{h}{2e}$


$$\begin{aligned} \frac{\partial \varphi}{\partial t} &= -\frac{1}{\hbar} \left( \frac{\hbar}{2m} (\cancel{j^2(-a)} - j^2(+a)) \right) - \frac{1}{\hbar} [g^* v(-a) - g^* v(+a)] - \frac{2\pi}{\Phi_0} \int_L^R \frac{\partial \bar{A}}{\partial t} \cdot d\bar{l} \\ &= \int_L^R \left[ \frac{g^*}{\hbar} \vec{\nabla} v - \frac{2\pi}{\Phi_0} \frac{\partial \vec{A}}{\partial t} \right] d\bar{l} = \frac{2\pi}{\Phi_0} \int_L^R \left[ -\vec{\nabla} v - \frac{\partial \vec{A}}{\partial t} \right] d\bar{l} = \frac{2\pi}{\Phi_0} \int_L^R \vec{E} \cdot d\bar{l} \end{aligned}$$

electric potential voltage difference  $V_L - V_R$

\* Circuit relations

$$\left. \begin{aligned} I &= \int_{\text{cross sect}} \vec{j} \cdot d\vec{s} \sim I_c \sin[\varphi(t)] \\ \frac{\partial \varphi}{\partial t} &= \frac{2\pi}{\Phi_0} \cdot V \sim \frac{2\pi}{\Phi_0} \cdot \frac{\partial}{\partial t} (\phi_L - \phi_R) \end{aligned} \right\}$$
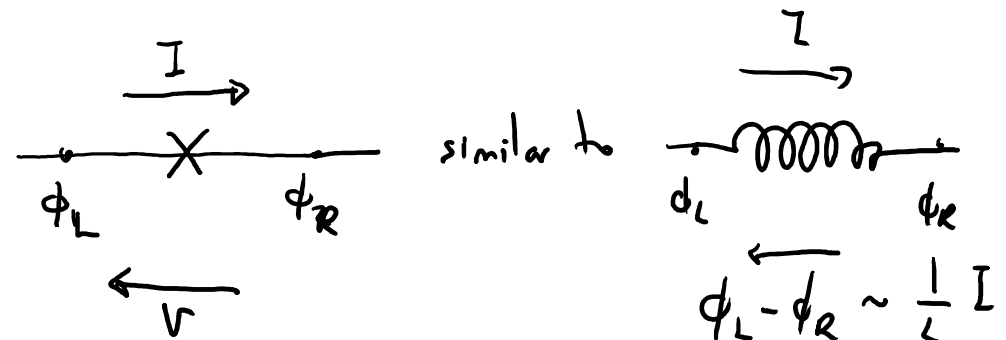
$$I = I_c \sin \left( \frac{2\pi}{\Phi_0} \cdot (\phi_L - \phi_R) \right)$$



# Fluxoid quantization (2)

Sunday, February 7, 2016 5:15 PM

Remember  $\frac{\hbar}{q^*} = \frac{\hbar}{-2e} = \frac{-\Phi_0}{2\pi}$

$$\oint_C (\nabla \theta) \cdot d\vec{l} = \oint_C \frac{\hbar}{q^*} \nabla \theta \cdot d\vec{l} - \oint_C \vec{A} \cdot d\vec{l}$$

$$\oint_{\gamma} (\nabla \theta) \cdot d\vec{l} \cdot \left( \frac{-2\pi}{\Phi_0} \right) = + \int_{\gamma} \nabla \theta \cdot d\vec{l} + \frac{2\pi}{\Phi_0} \int_{\gamma} \vec{A} \cdot d\vec{l}$$

$$\oint_{\gamma} \nabla \varphi \equiv + \oint_{\gamma} \nabla \theta \cdot d\vec{l} - \frac{2\pi}{\Phi_0} \oint_{-\gamma} \vec{A} \cdot d\vec{l}$$


} closed paths

$$\frac{\Phi_0}{2\pi} \oint_C \nabla \varphi \cdot d\vec{l} = \Phi_0 \times \mathbb{Z} + \left( \int_{In(C)} \vec{B} \cdot d\vec{s} \right) = \Phi_{ext}$$

Through phase-flux relation

$$\phi = \frac{\Phi_0}{2\pi} \cdot \varphi$$
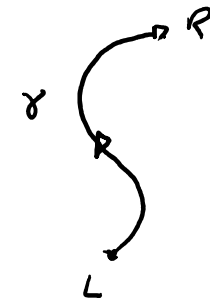
$$\oint_C \nabla \phi \cdot d\vec{l} = \Phi_{ext} = \Phi_0 \cdot m \quad (m \in \mathbb{Z})$$



$\gamma$  is a directed path between two points

We take "L" to be an origin for the phase


$\Leftarrow$  Definition of gauge invariant phase

# Conventions


Sunday, February 7, 2016 7:31 PM

\* Current is regarded in terms of positive charges.

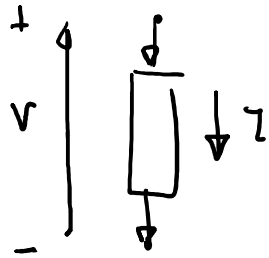\* Such carriers flow from large to small electric potential



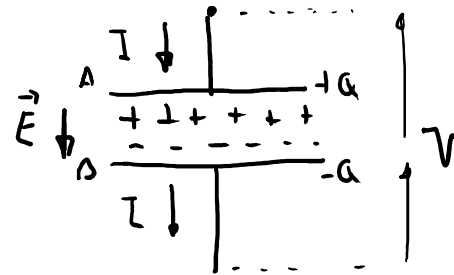\* On a capacitor, current flows lead to charge accumulation and establishment of a potential difference



\* Note that the sense of the flow that charges the capacitor is opposite to that of the established  $V$

$$I = \frac{dQ}{dt} = C \dot{V}$$

\* Note also that  $V = \int_a^b E dx$


\* On an inductor, a growth of current induces a potential that opposes the current (Lenz's law)



$$V = L \frac{dI}{dt}$$


# Applying the convention

Sunday, February 7, 2016 8:40 PM

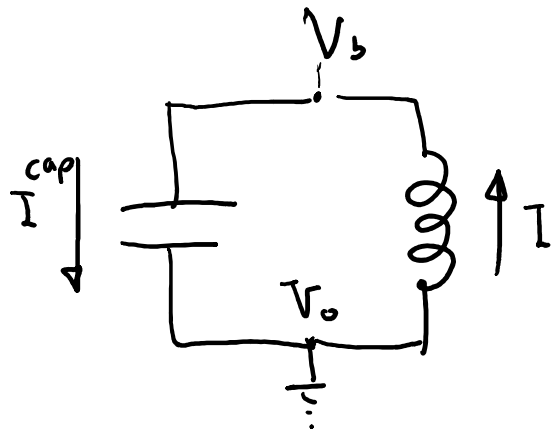


\* The sum of the currents going into capacitive elements must be equal to the sum of currents coming from inductive elements
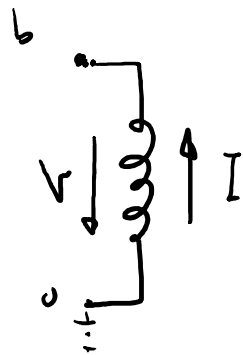
$$I_{b \rightarrow o}^{cap} = I_{o \rightarrow b}^{ind}$$



$$V_o - V_b = L \frac{dI}{dt}$$

$$\int (V_o - V_b) dt = LI$$

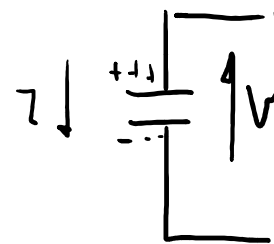

$$(V_b - V_o) \cdot C = Q$$

$$(\dot{V}_b - \dot{V}_o) C = I$$

flux variable:

$$\frac{\phi_o - \phi_b}{L} = (\ddot{\phi}_o - \ddot{\phi}_b) C \Rightarrow \ddot{\phi}_b = -\frac{1}{LC} \phi_b$$

$\phi_o = 0$   
grounded

# Detailed rules

Tuesday, February 9, 2016 11:07 AM


- 1) Draw the graph for your circuit and assign nodes to the intersections or connections
- 2) Define one flux variable for each node
- 3) Draw a directed subgraph (tree) starting from one node and running over all
- 4) Define branch fluxes as the flux difference between consecutive nodes on that tree
- 5) Assign branch fluxes to the remaining branches that close loops using fluxoid

quantization  $\sum_{\text{loop}} \delta\phi = \Phi_{\text{ext}} \quad (+ 2\pi m \Phi_0 \approx 0)$

- 6) Write differential equations for each node

$$\sum \text{currents} = 0$$

- 7) Find Lagrangian and quantize

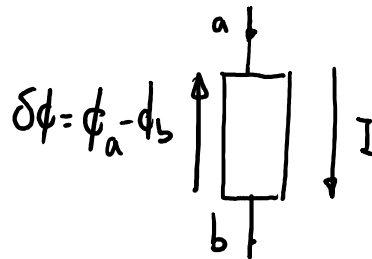

1. Capacitor  $I = C \delta\ddot{\phi}$


2. Inductor  $I = \frac{1}{L} \delta\phi$

3. Junction  $I = \frac{\Phi_0}{L_j} \sin(\delta\phi)$



# Driven capacitor

Tuesday, February 9, 2016 11:16 AM

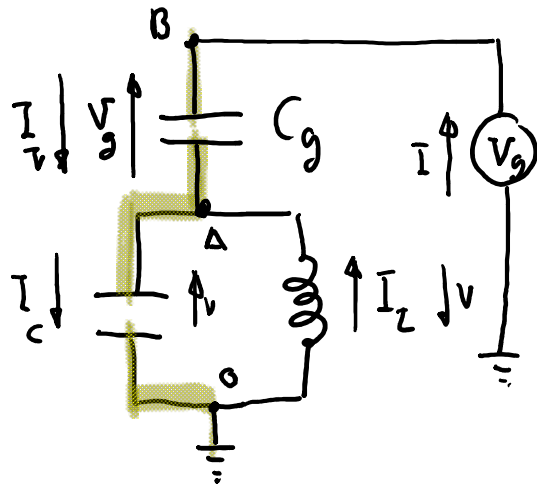

$$I_c - I_L = I_v$$

$$I_c = C (\ddot{\phi}_A - \ddot{\phi}_o)$$

$$I_v = C_g (\ddot{\phi}_B - \ddot{\phi}_A)$$

$$I_L = \frac{1}{L} (\phi_o - \phi_A)$$

We assume

- 1) No trapped fluxes
- 2) Grounded circuit  $\phi_o = 0$
- 3) Constant voltage due to source  $V_g \Rightarrow \dot{\phi}_B = V_g$

$$C \ddot{\phi}_A + \frac{1}{L} \phi_A = C_g (\dot{V}_g - \ddot{\phi}_A)$$

$$\frac{d}{dt} \left[ (C + C_g) \left( \dot{\phi}_A - \frac{C_g}{C + C_g} V_g \right) \right] = -\frac{1}{L} \phi_A$$


$$\mathcal{L} = \frac{1}{2} C_\Sigma \left( \dot{\phi}_A - \frac{C_g}{C_\Sigma} V_g \right)^2 - \frac{1}{2L} \phi_A^2$$

$$q = C_\Sigma \dot{\phi}_A - C_g V_g$$

$$\mathcal{H} = \frac{1}{2C_\Sigma} \left( q + \underbrace{\frac{C_g}{C_\Sigma} V_g}_{q_g} \right)^2 + \frac{1}{2L} \phi_A^2$$

# Driven capacitor (2)

Tuesday, February 9, 2016 6:00 PM

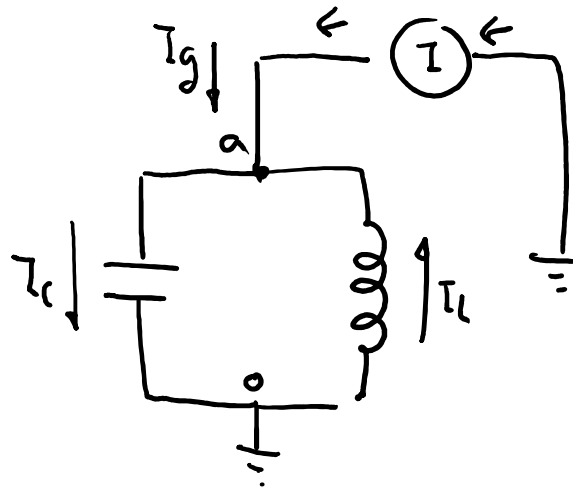

$$\left. \begin{aligned} I_c - I_L &= I_g \\ I_c &= C (\ddot{\phi}_A - \ddot{\phi}_o) \\ I_L &= \frac{1}{L} (\phi_o - \phi_A) \end{aligned} \right\}$$

$$C \ddot{\phi}_A = -\frac{1}{L} \phi_A + I_g$$

$$\mathcal{L} = \frac{1}{2} C (\dot{\phi}_A)^2 - \frac{1}{2L} (\phi_A - LI_g)^2 + \text{constants}$$

$$\mathcal{H} = \frac{1}{2C} q^2 + \frac{1}{2L} (\phi_A - LI_g)^2$$